

date: 2024-01-26

# TFE4188 - Lecture 3



## Reference and bias


# Goal for today

Understand **why** we need reference and bias circuits


Introduction to **circuit architectures**

**W w h y**

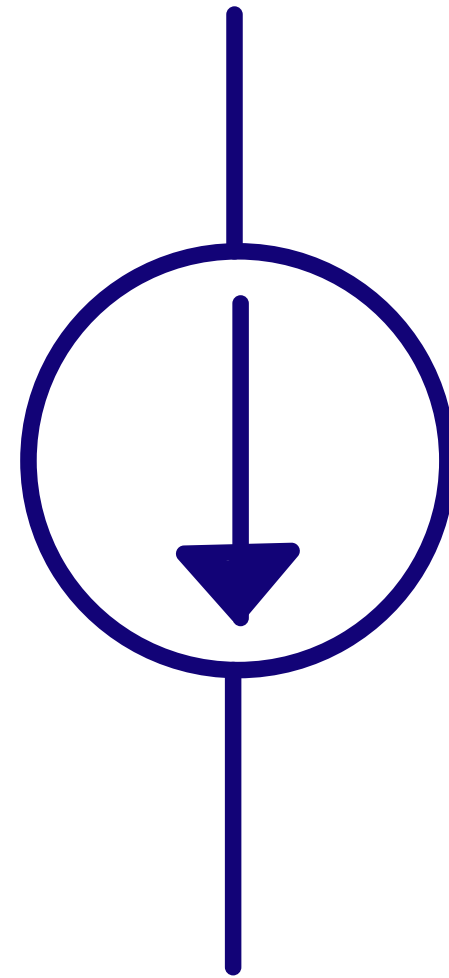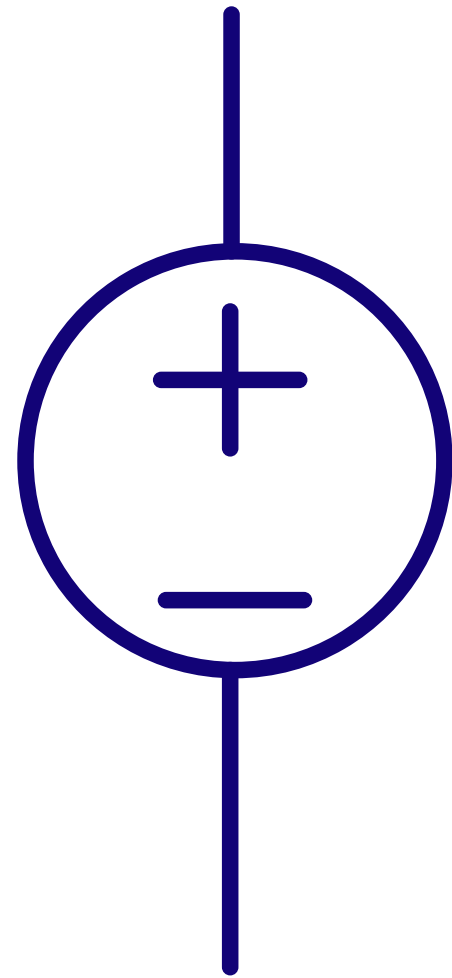

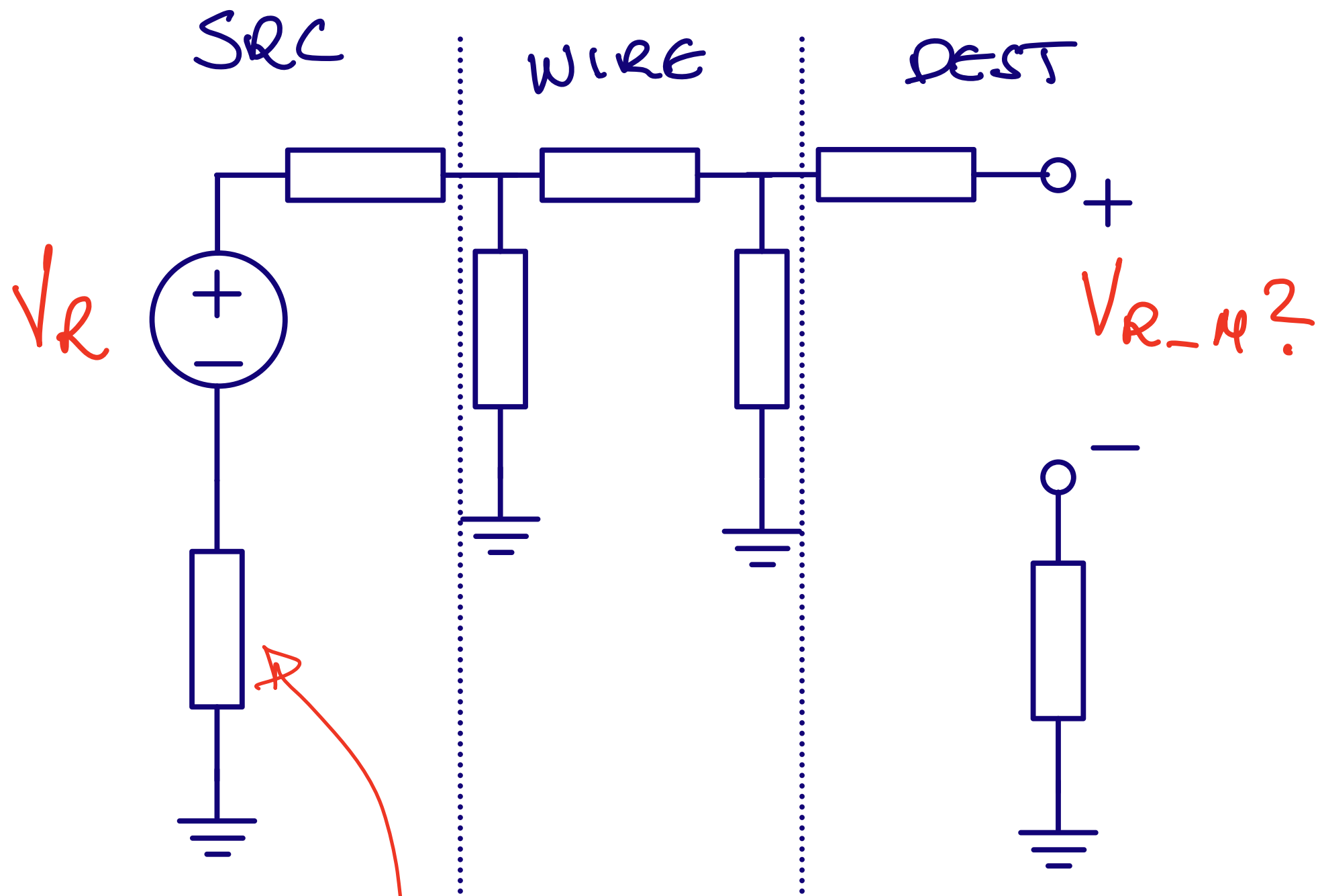


$$Z(t, V, f, T, P)$$

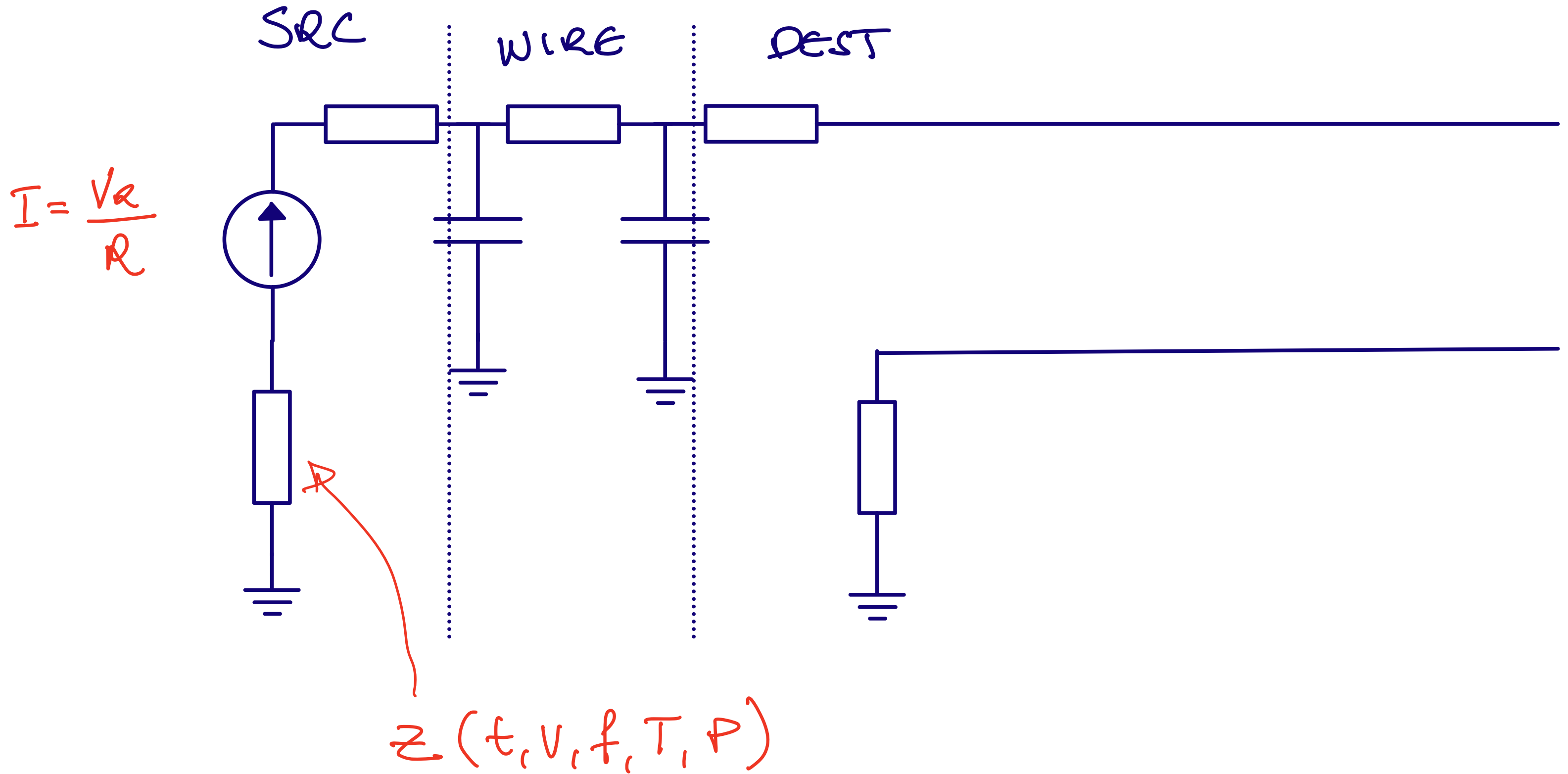
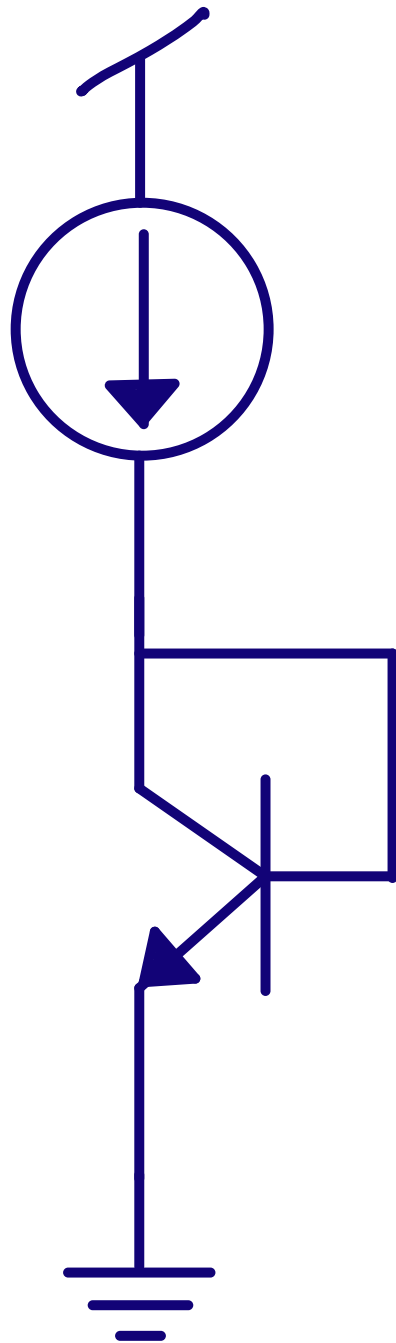
# Bandgap voltage reference

A voltage complementary to temperature (CTAT)



$$I_D = I_S \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) + I_B \approx I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_T = \frac{kT}{q}$$

$$V_{BE} = \frac{kT}{q} \ln \frac{I_C}{I_S}$$



$$I_S = qA n_i^2 \left[ \frac{D_n}{L_n N_A} + \frac{D_p}{L_p N_D} \right]$$




Some algebra (see [Diodes](#))

$$V_{BE} = \frac{kT}{q} (\ell - 3 \ln T) + V_G$$
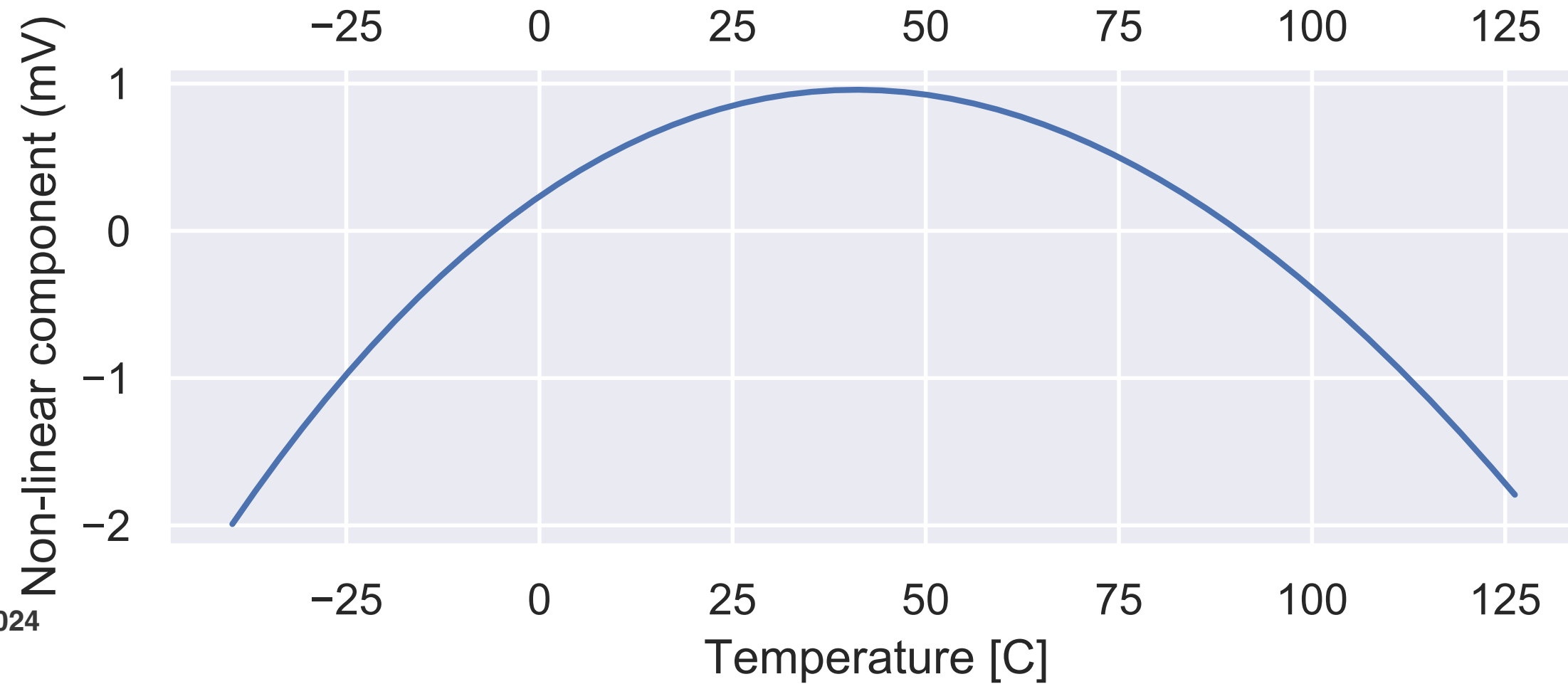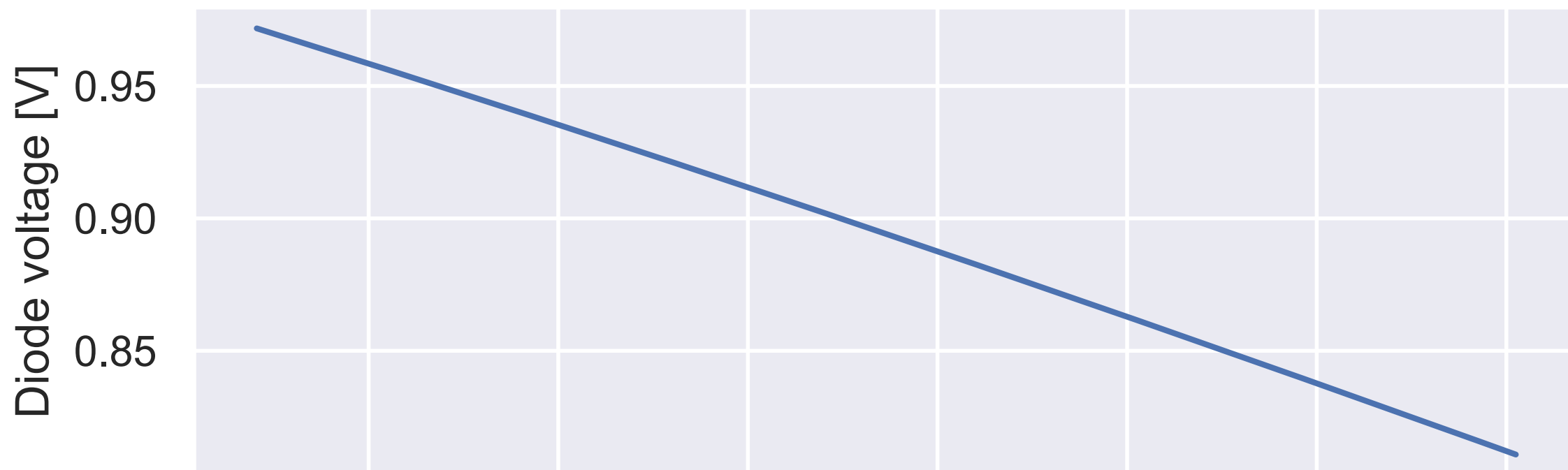
$$\ell = \ln I_C - \ln qA - \ln \left[ \frac{D_n}{L_n N_A} + \frac{D_p}{L_p N_D} \right] - 2 \ln 2 - \frac{3}{2} \ln m_n^* - \frac{3}{2} \ln m_p^* - 3 \ln \frac{2\pi k}{h^2}$$




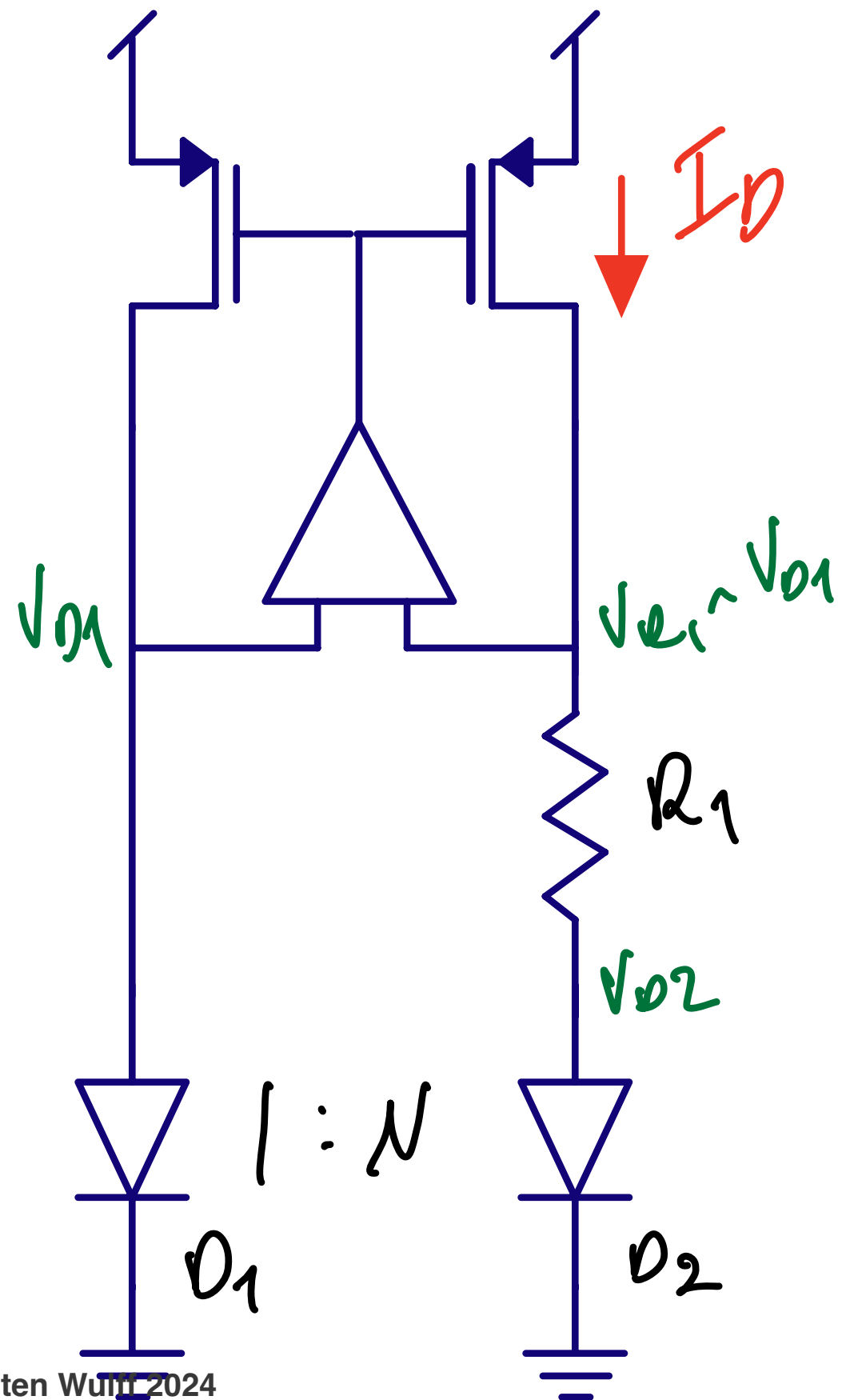
A current proportional to temperature (PTAT)




$$V_{D1} - V_{D2} = V_T \ln \frac{I_D}{I_{S1}} - V_T \ln \frac{I_D}{I_{S2}} = V_T \ln \frac{I_{S2}}{I_{S1}} = V_T \ln N$$

How to combine a CTAT with a PTAT ?

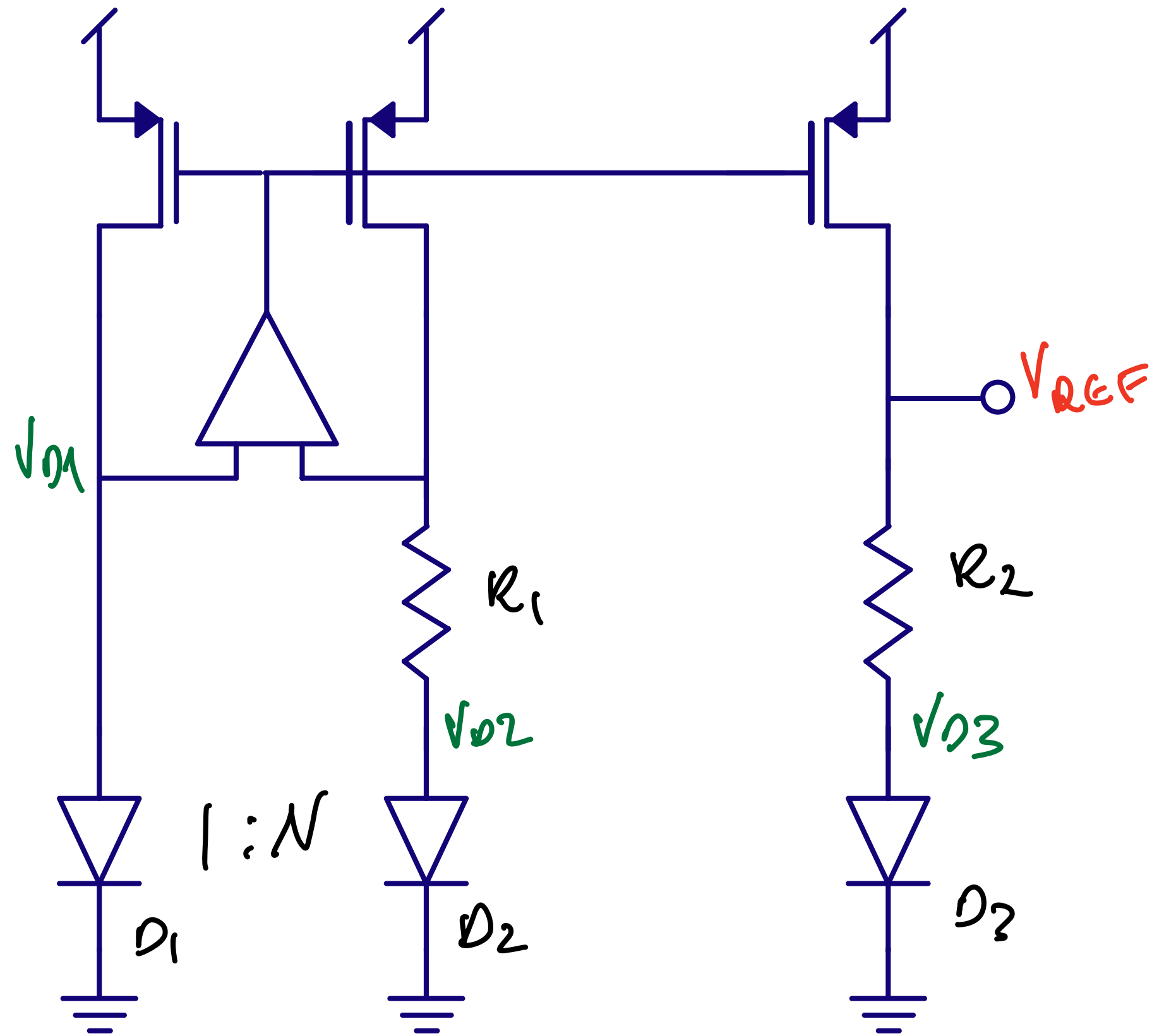


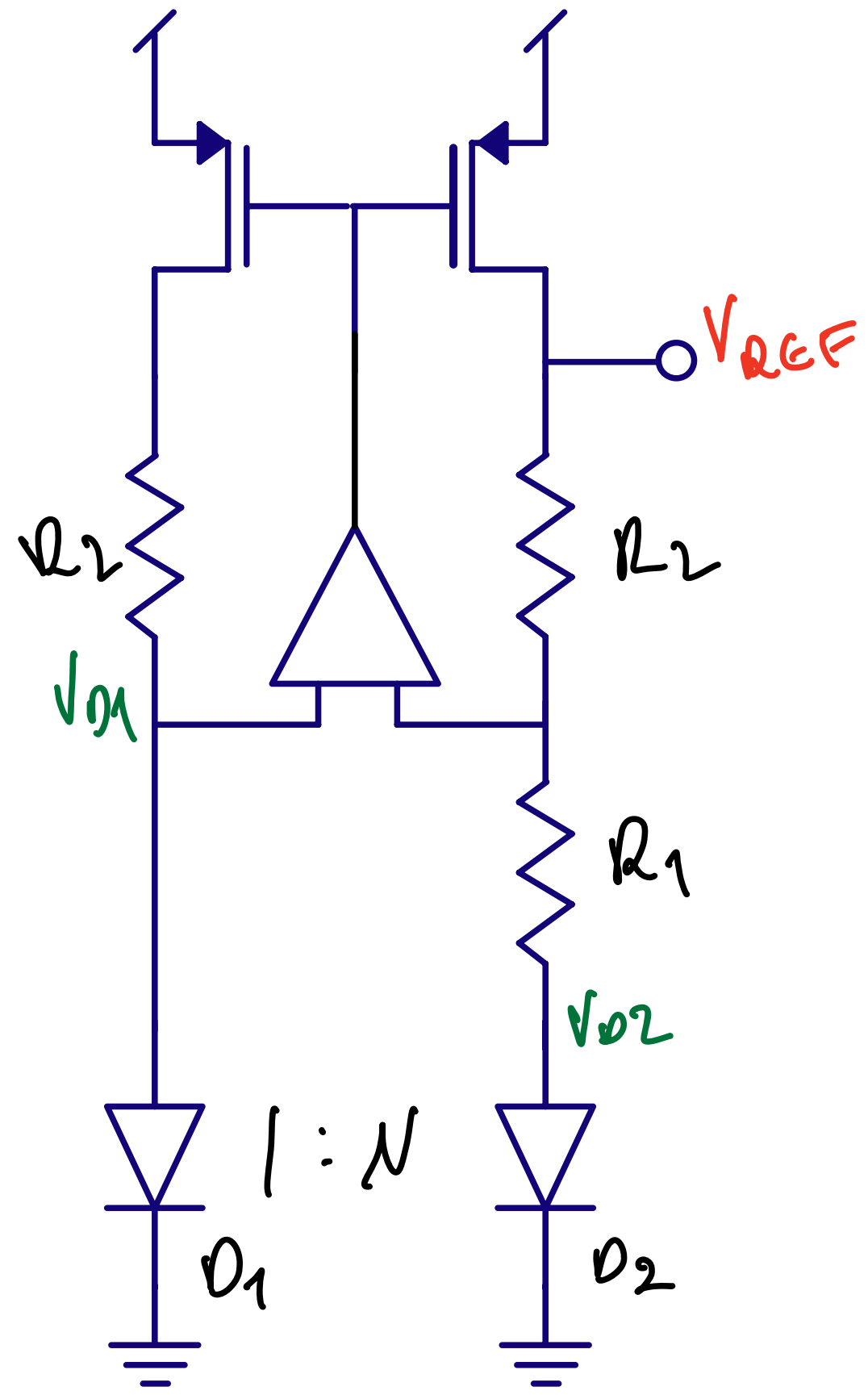


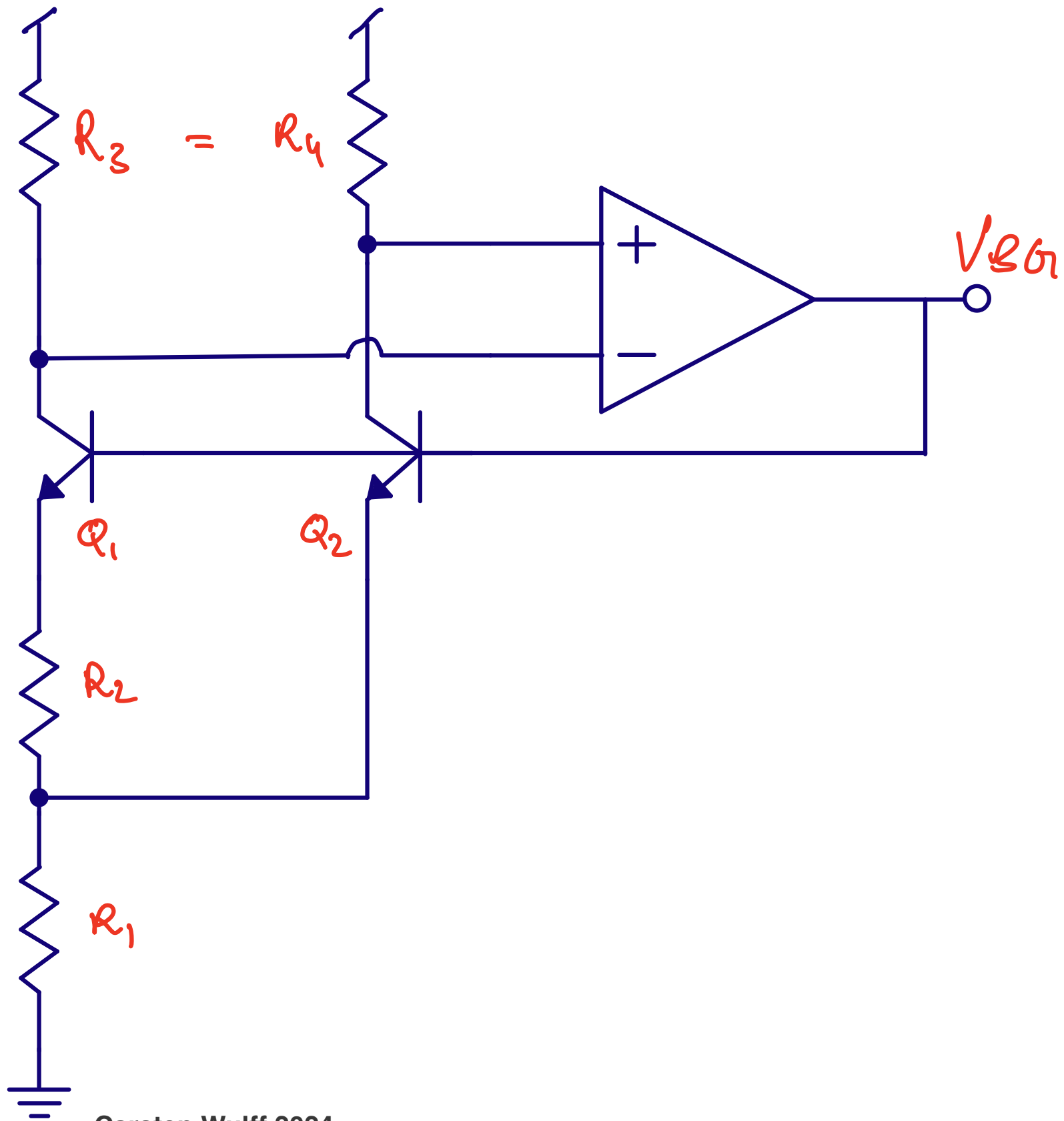


$$V_{BG} = V_{G0} + (m - 1) \frac{kT}{q} \ln \frac{T_0}{T} + T \left[ \frac{k}{q} \ln \frac{J_2}{J_1} \frac{2R_2}{R_1} - \frac{V_{G0} - V_{be0}}{T_0} \right]$$


■ w\_vref    👁 typical

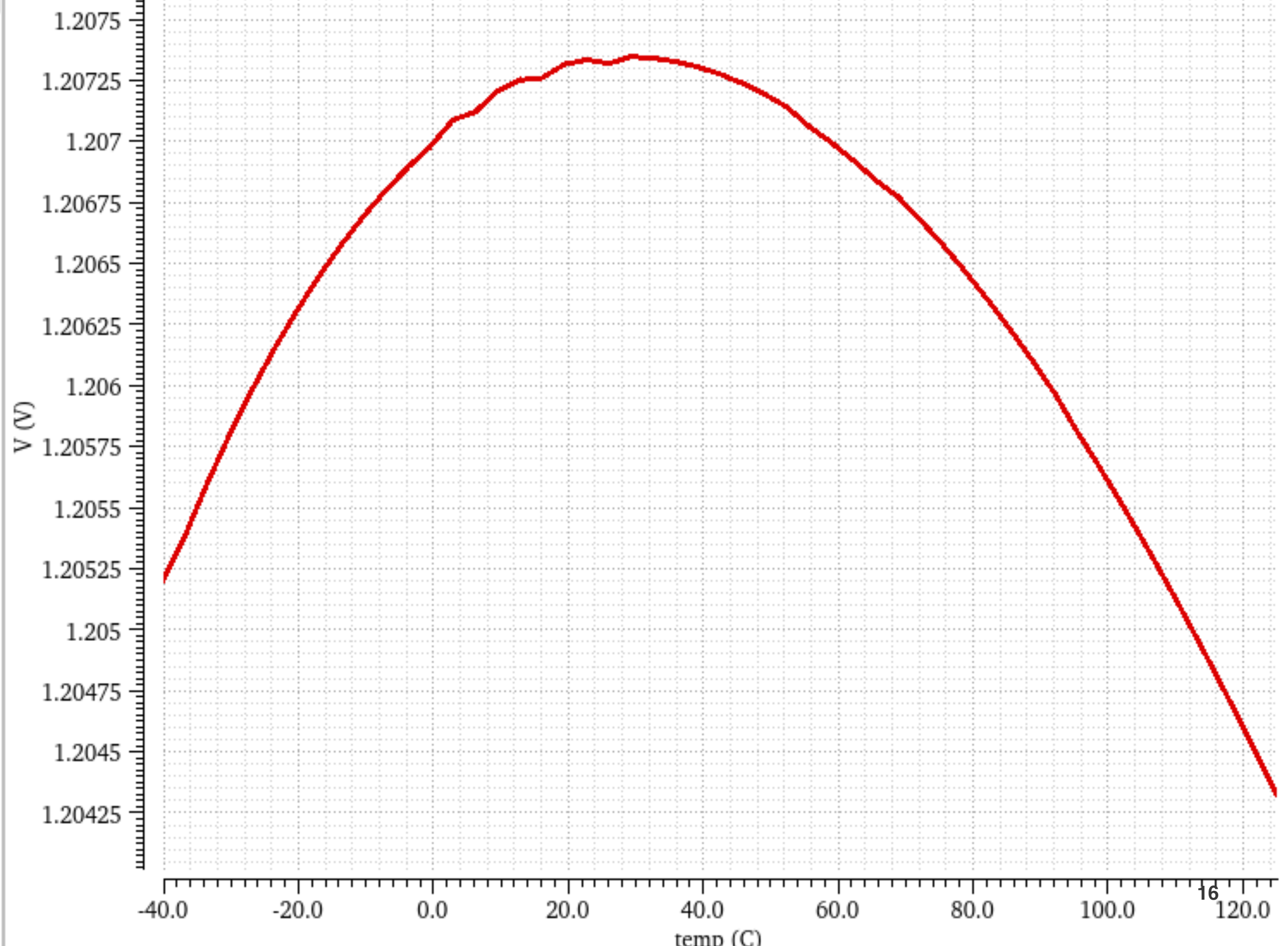




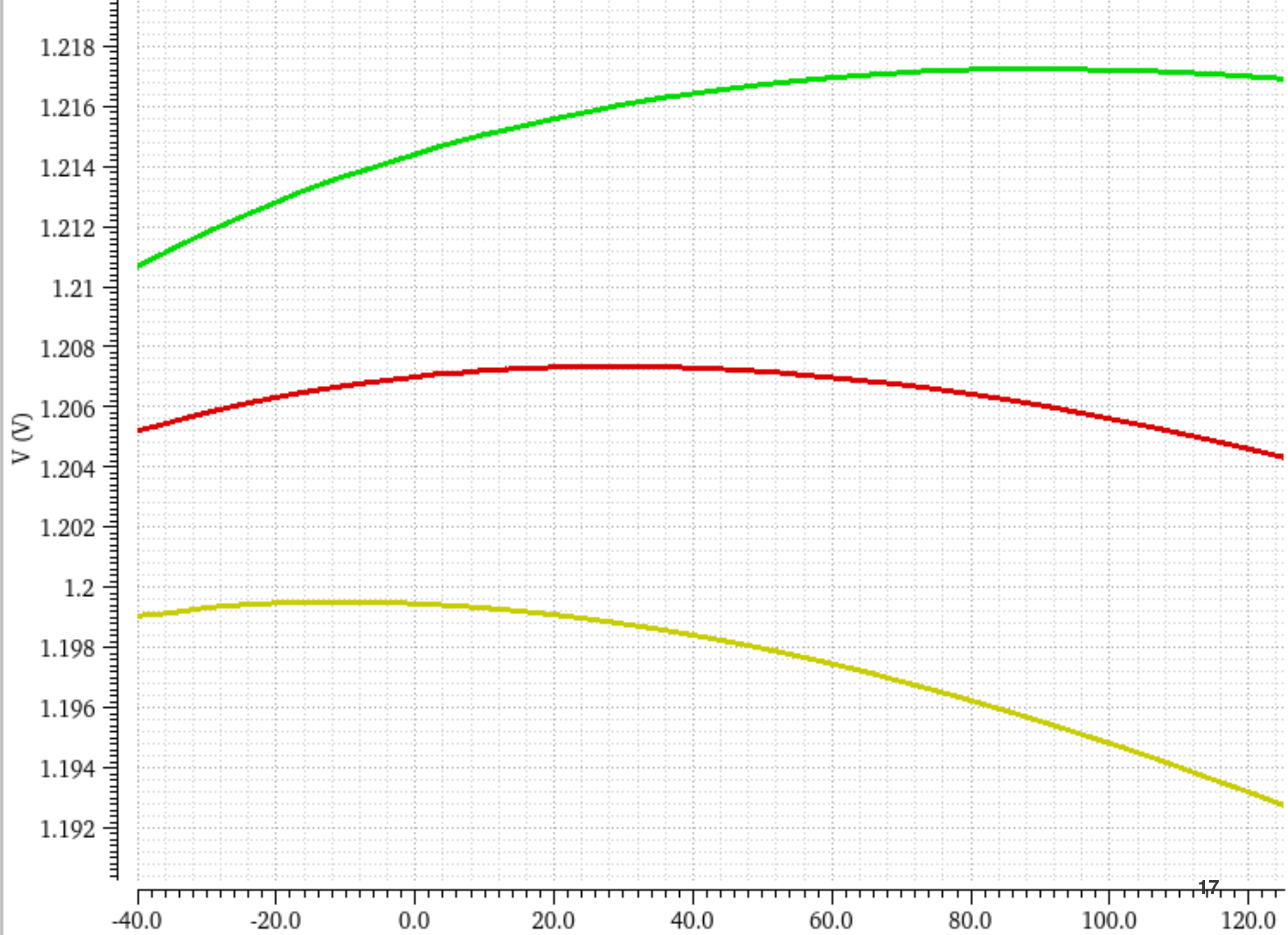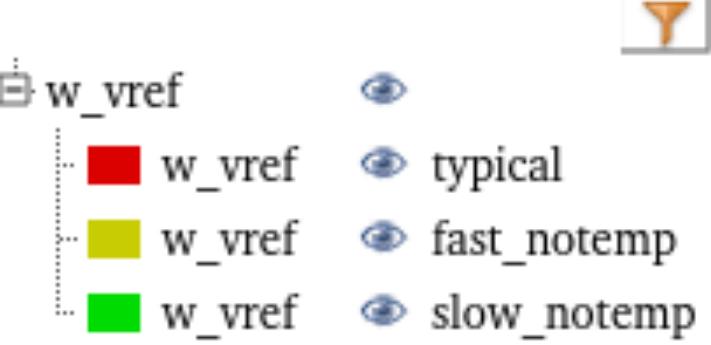



# Low voltage bandgap

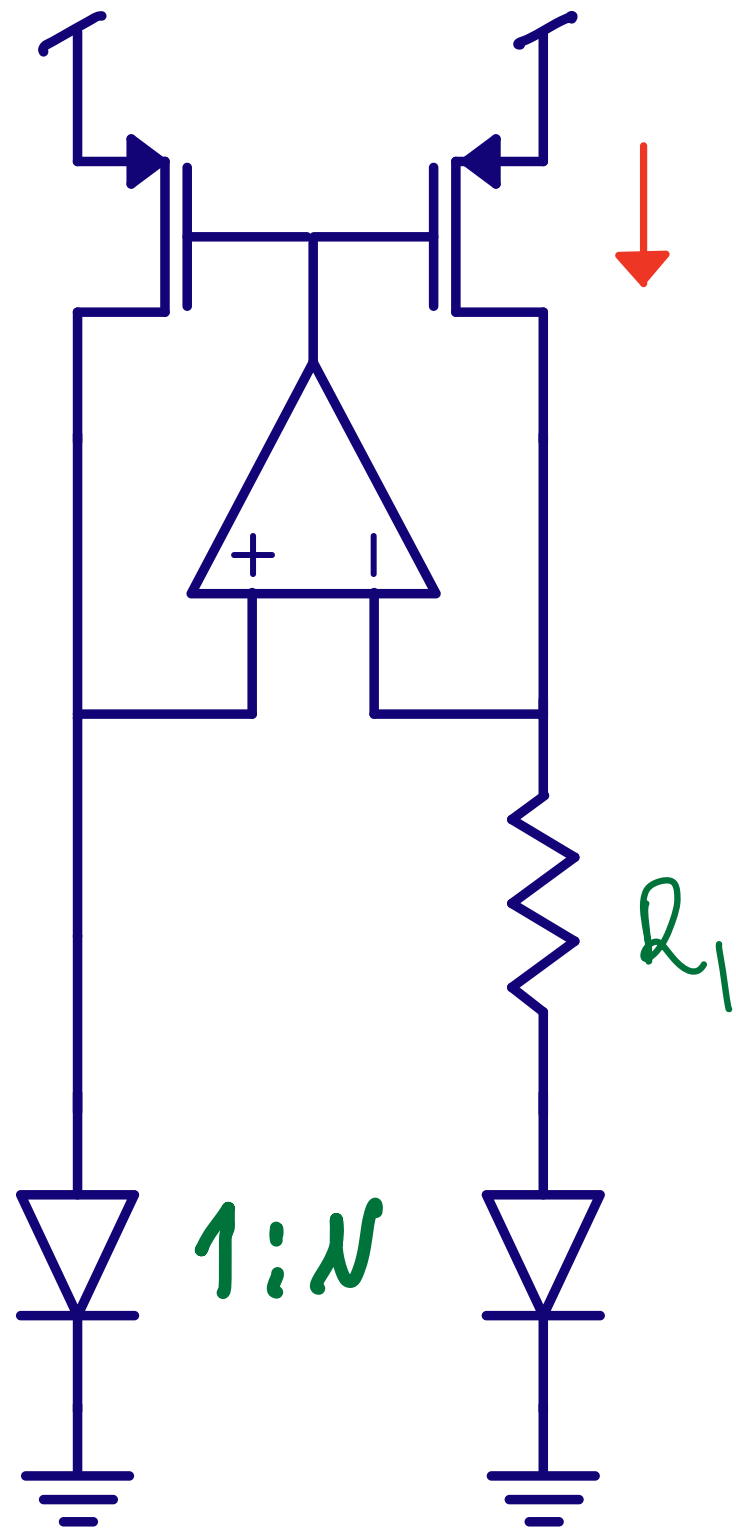

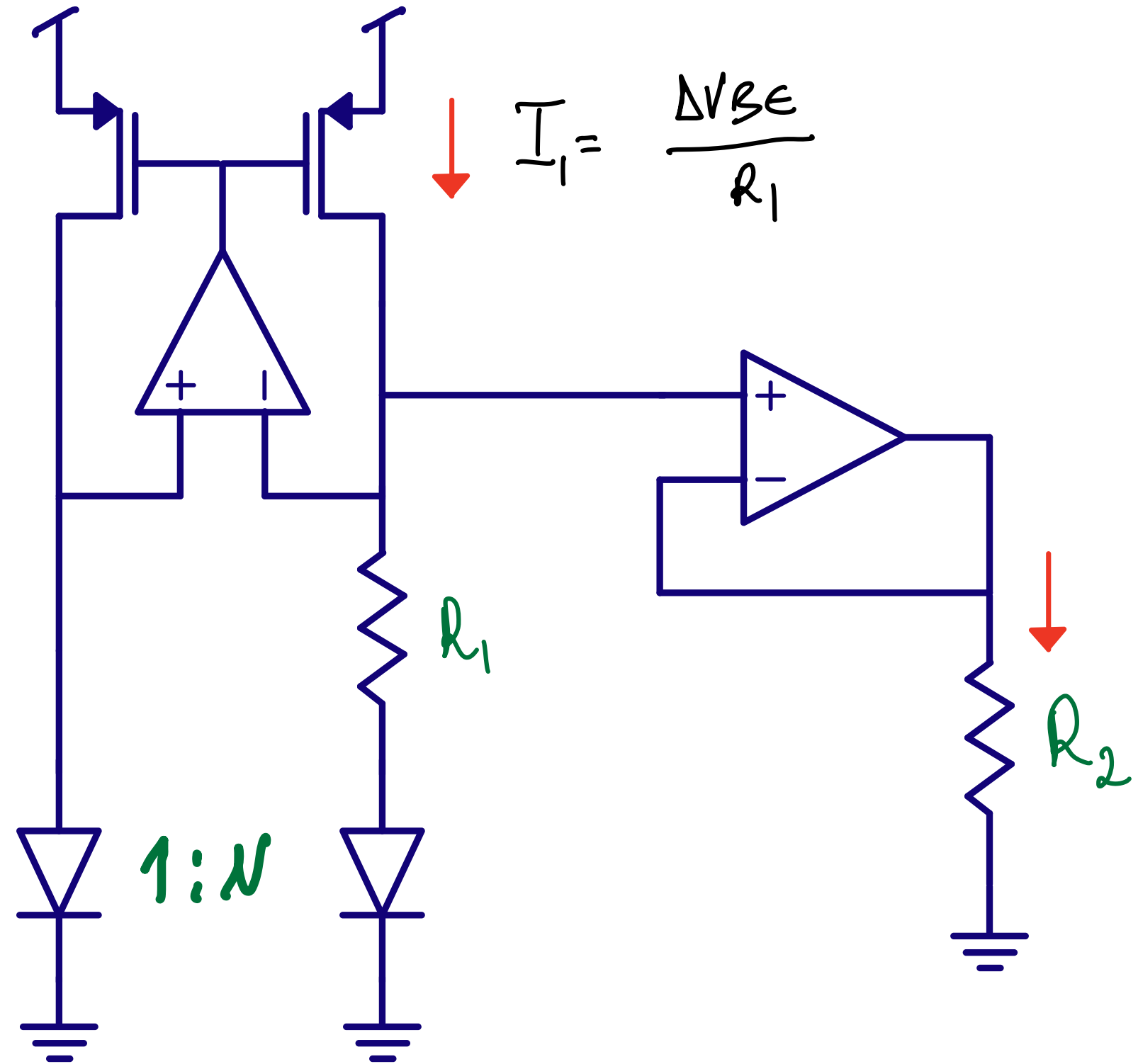
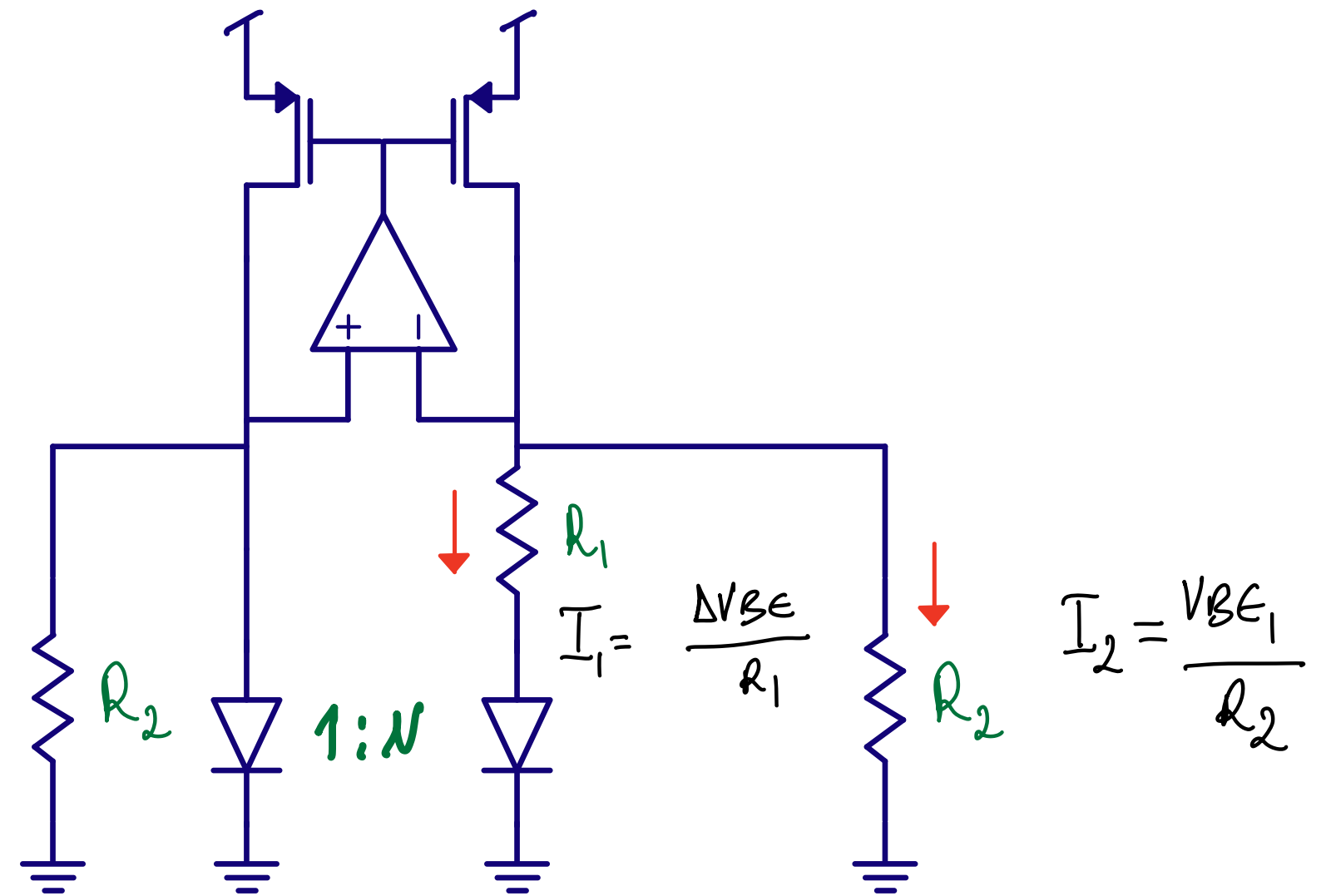
$$I_{PMOS} = \frac{V_D}{R_2} + \frac{\Delta V_D}{R_1}$$




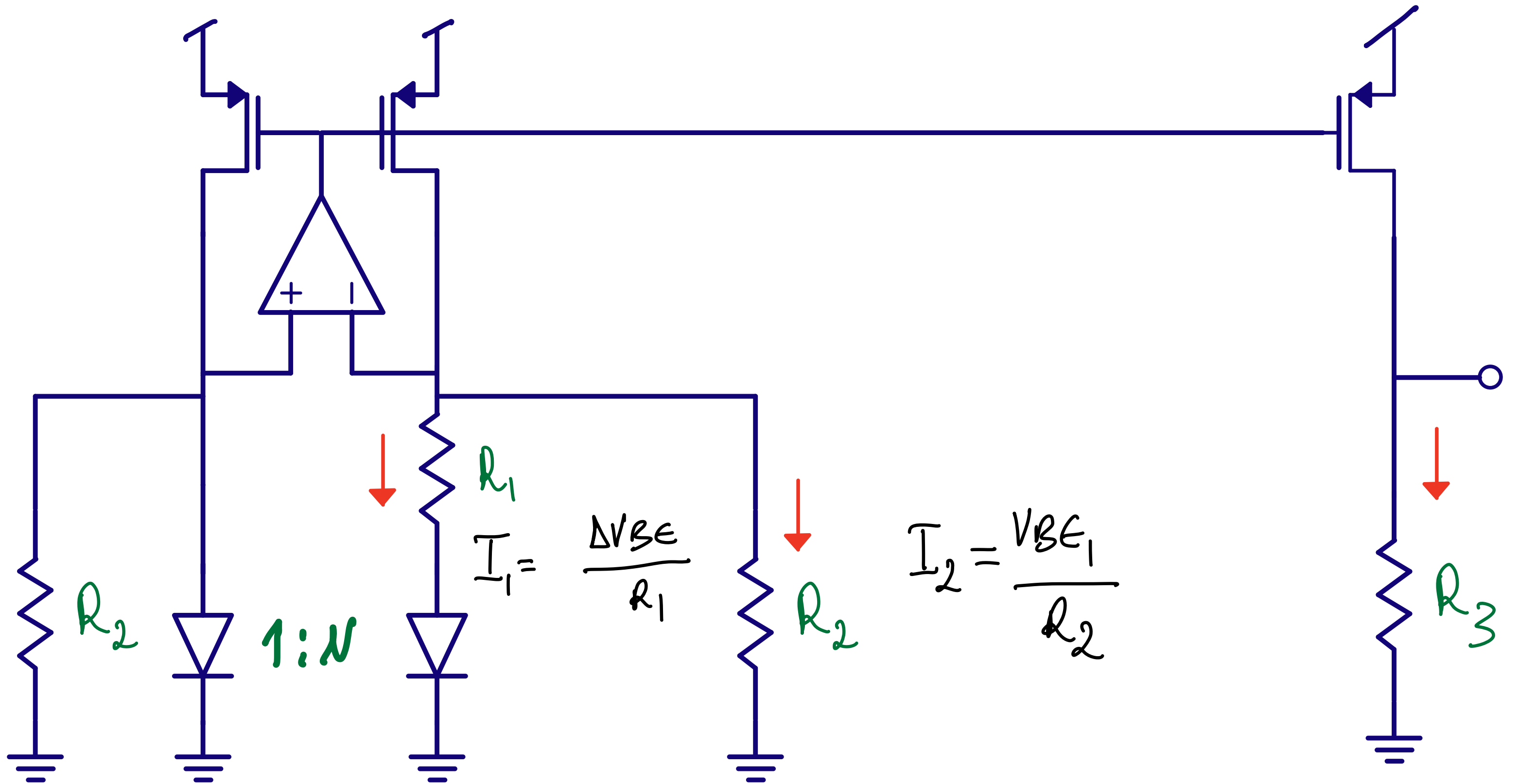


# Bias

Sometimes we just need a current




# How does a VI converter circuit work?

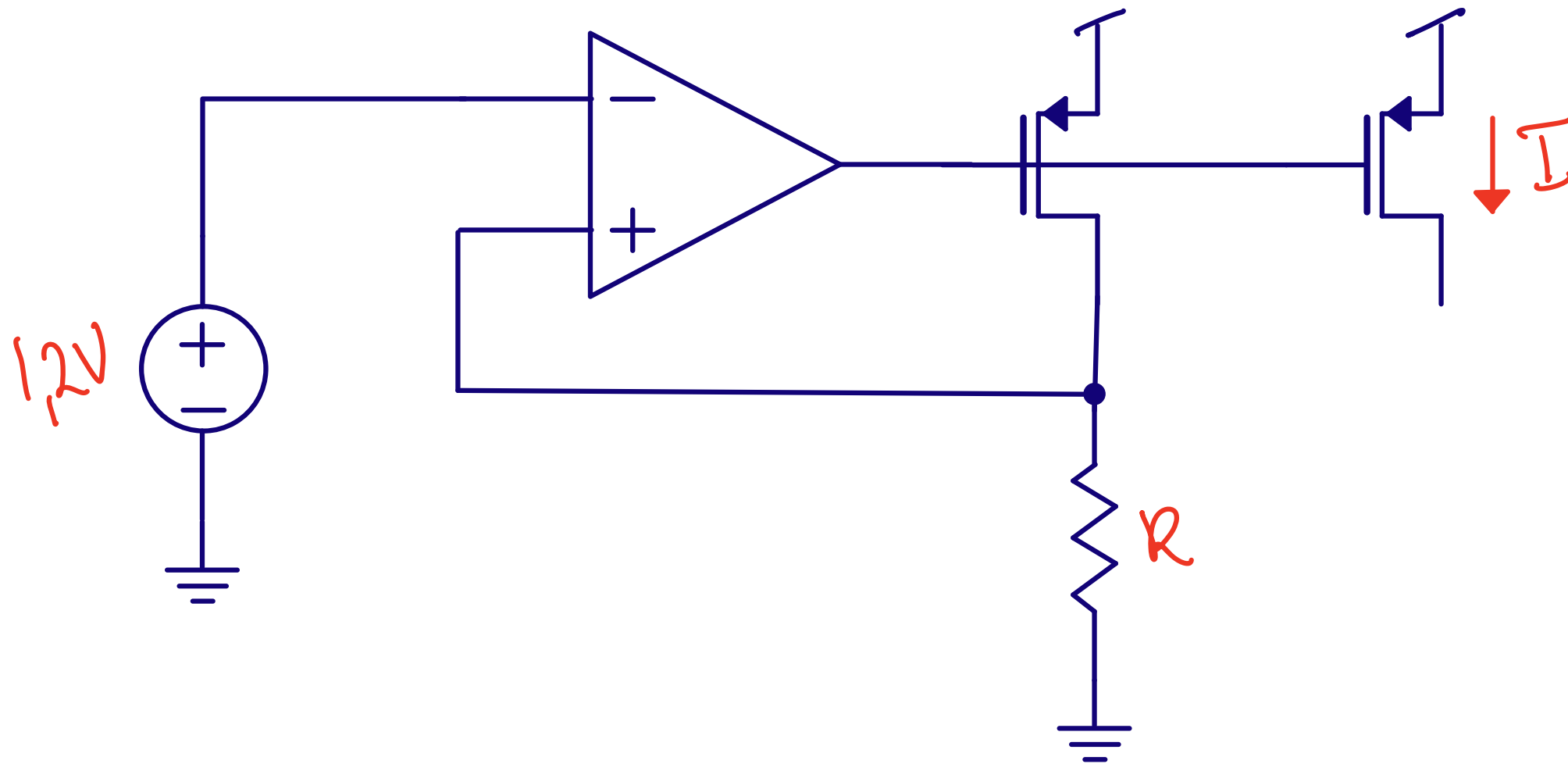



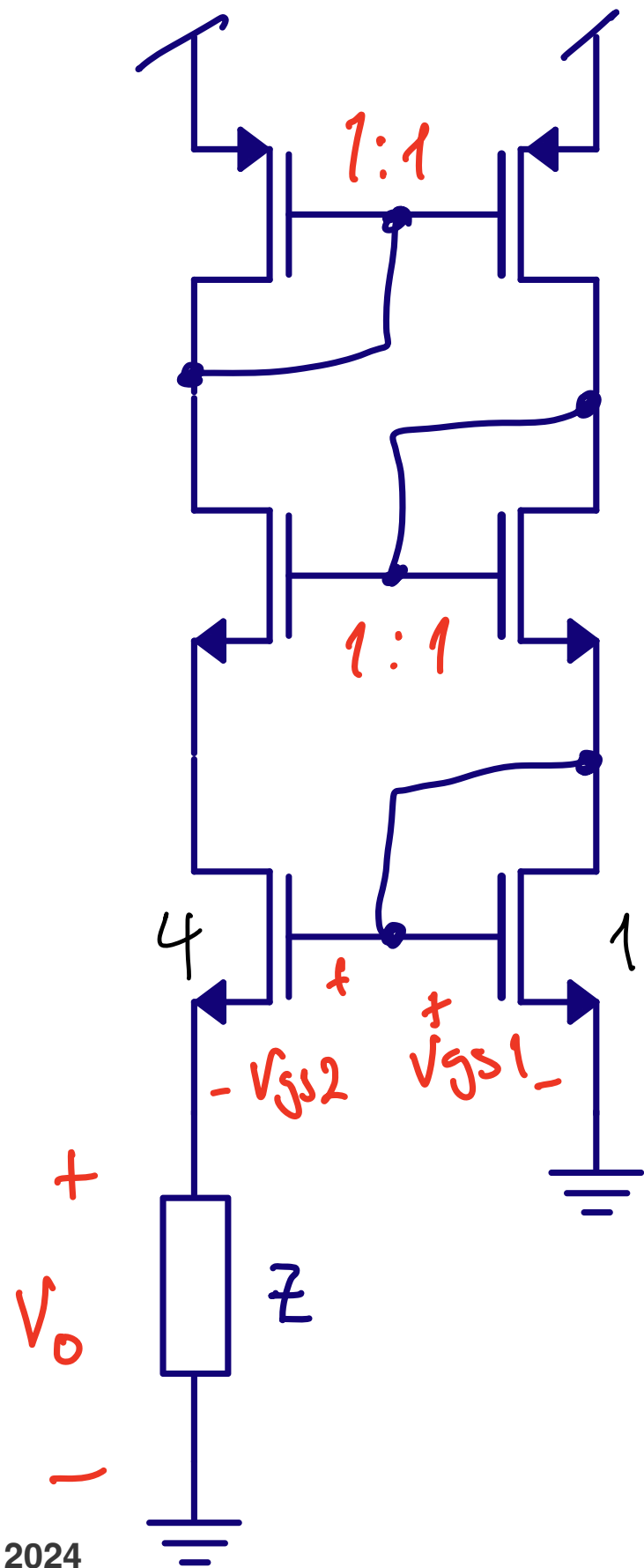

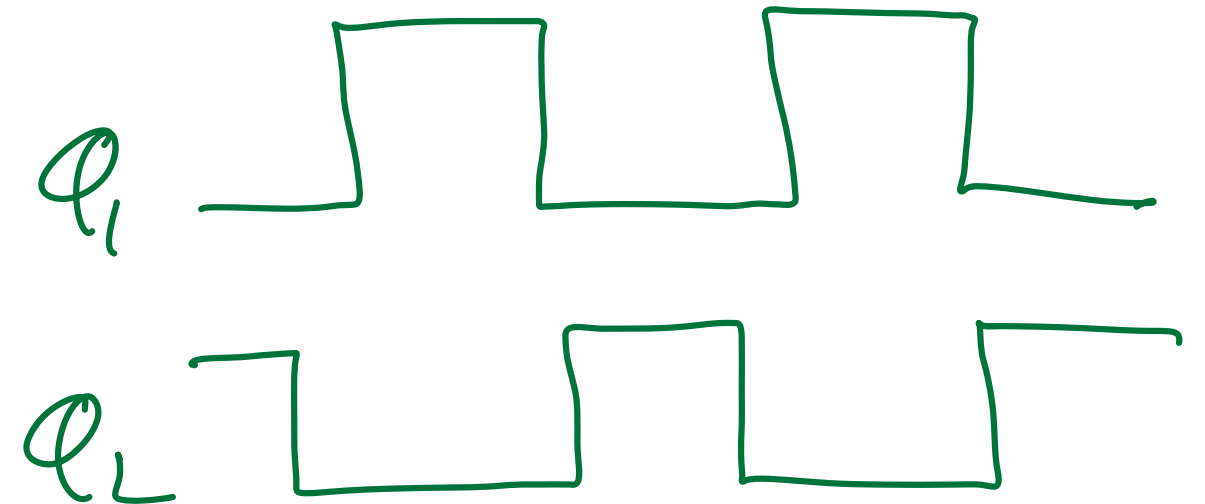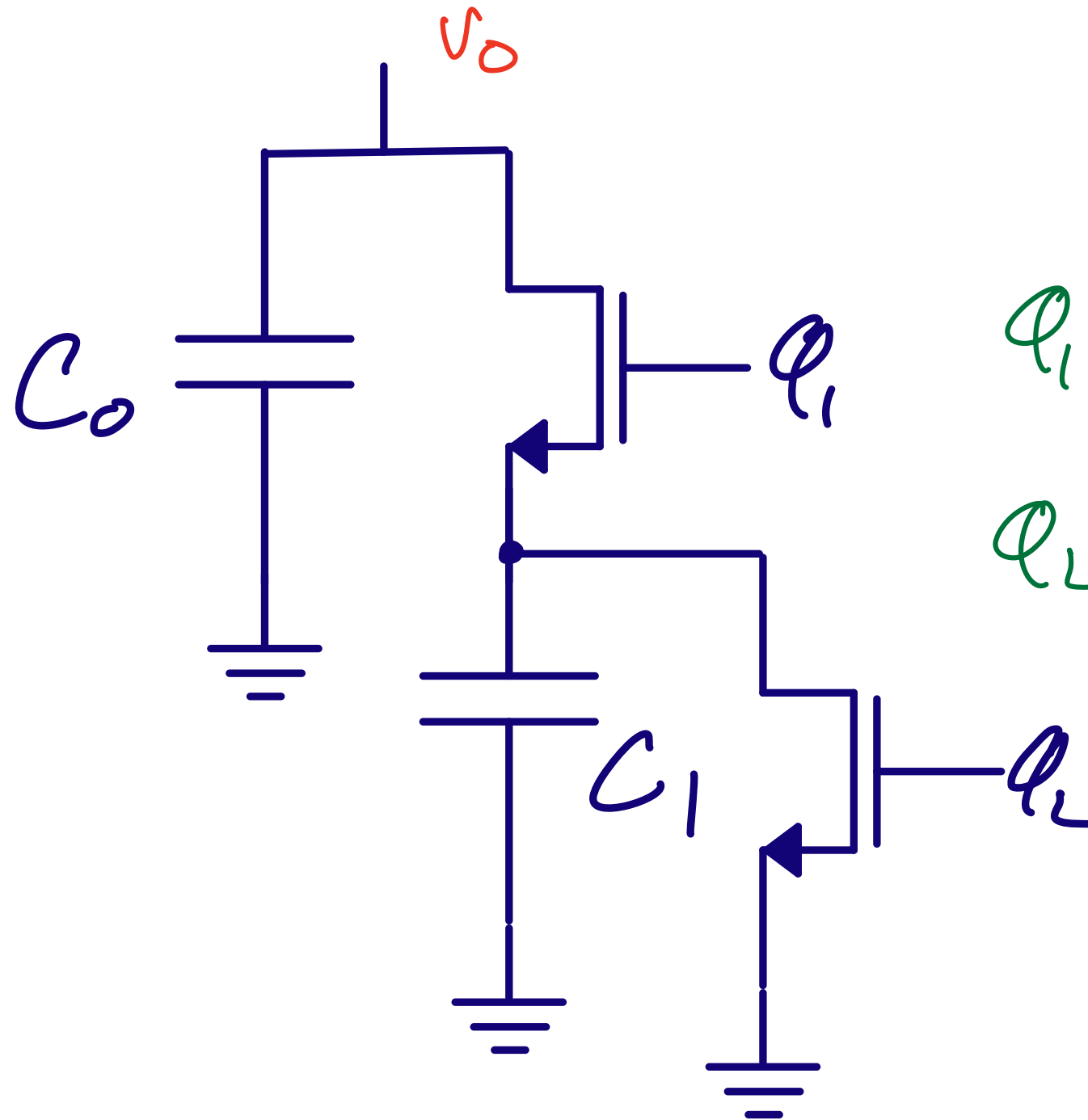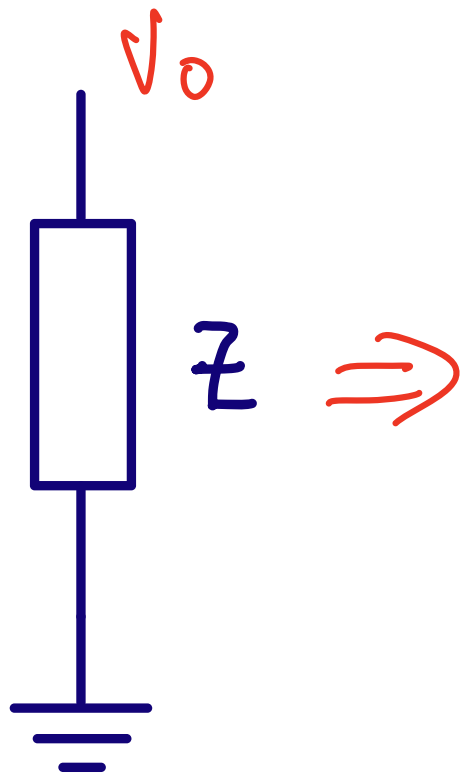GmCell: Why is  $1/Z$   
 proportional to  
 transistor  
 transconductance?



**Thanks!**

